

Now that we are familiar with the individual logic gates and their truth conditions we are in a position to create **logic circuits**. These are combinations of logic gates controlled by inputs that can provide a range of useful outputs.

## Basic example

In the below circuit we have the following gates connected to two inputs with one output, moving through the following stages:

1. AND, NOT , NOT
2. AND, NOR


This is equivalent to the following truth table:

A	B	Output	
-	-	-----	
0	0	0	(1)
1	0	1	(2)
0	1	1	(3)
1	1	0	(4)



*Line 1 of the truth table*



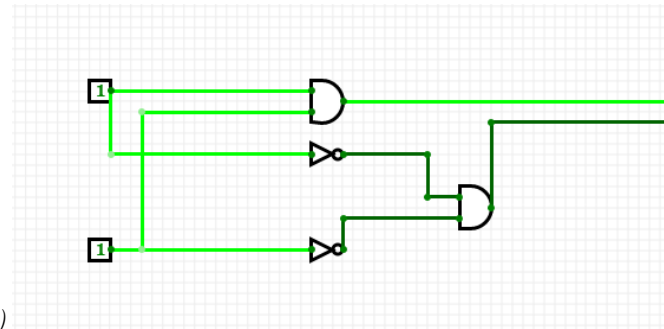

Line 2 and 3 of the truth table (equivalent to each other)

Line 4 of the truth table

## Applied example

With this circuit we have a more interesting applied example.

It corresponds to an automatic sliding door and has the following states

- a proximity sensor that opens the doors when someone approached from outside
- a proximity sensor that opens the doors when someone approaches from the inside
- a manual override that locks both approaches (inside and out) meaning no one can enter or leave

Here's a visual representation: [! logic\\_circuits\\_5.gif](#) The following truth table represents this behaviour, with A and B as the door states, C as the override and X as the door action (0 = open, 1 = closed)

A	B	C	X
-	-	-	-
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	1
0	1	1	1
1	1	1	1



*Automatic door sensor with manual override*